



"SOLO-PRO" WIRING DIAGRAM

Designed by Paul J. Marossy 7/5/04 Revised 1/17/05

This simple little circuit allows you to switch between two preset volume levels for easy access to a passive volume boost when soloing. All you have to do is step on the button! The two 0.001uF film caps are to help prevent the loss of highs if the volume control is turned down very low. These caps allow some of the highs to be bypassed directly to the output.